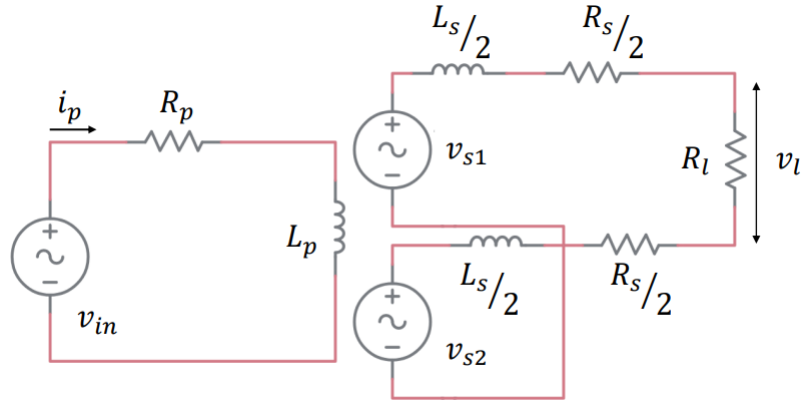


## Question 2




Given the LVDT, the output  $v_o(t)$  and input  $v_p(t)$  voltages are given by:

$$v_o(t) = k.x.\sin(\omega_p t + \phi)$$

$$v_p(t) = \sin(\omega_p t)$$

And  $L_p = 4mH$ ,  $L_s = 2mH$ ,  $R_p = 100\Omega$ ,  $R_s = 50\Omega$  find the output impedance and the frequency  $\omega_p$  at which  $\phi < 0.1\pi$

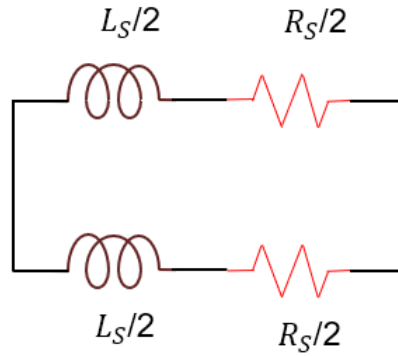To find the output impedance, we have to short the voltage sources and open the load resistance



Output impedance is given by:

$$Z = \sqrt{R_s^2 + X_L^2}$$

$$Z = \sqrt{R_s^2 + (j\omega L_s)^2}$$

$$Z = \sqrt{R_s^2 - \omega^2 L_s^2}$$

Therefore:

$$\phi = \tan^{-1} \frac{R_s}{\omega L_s}$$

Since we know that  $\phi < 0.1\pi$ , we can solve for  $\omega_p$ :

$$\omega_p < \frac{R_s}{L_s} \tan(0.1\pi)$$

$$\omega_p < 8122.99 \text{ rad/s}$$