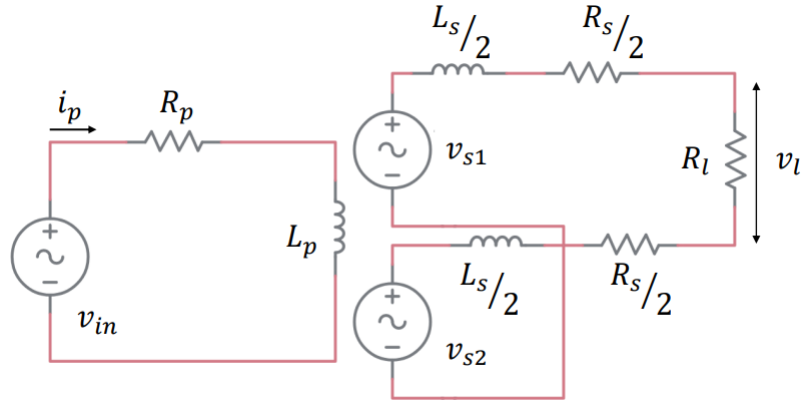


## Question 2




Given the LVDT, the output  $v_o(t)$  and input  $v_p(t)$  voltages are given by:

$$v_o(t) = k.x.\sin(\omega_p t + \phi)$$

$$v_p(t) = \sin(\omega_p t)$$

And  $L_p = 4mH$ ,  $L_s = 2mH$ ,  $R_p = 100\Omega$ ,  $R_s = 50\Omega$  find the output impedance and the frequency  $\omega_p$  at which  $\phi < 0.1\pi$

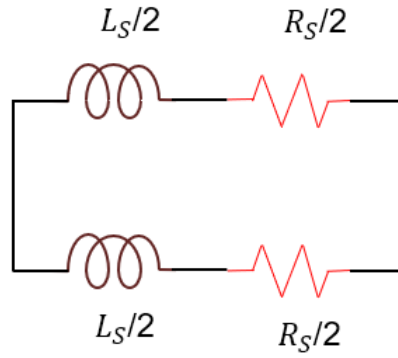To find the output impedance, we have to short the voltage sources and open the load resistance



Output impedance is given by:

$$Z = \sqrt{R_s^2 X_s^2}$$